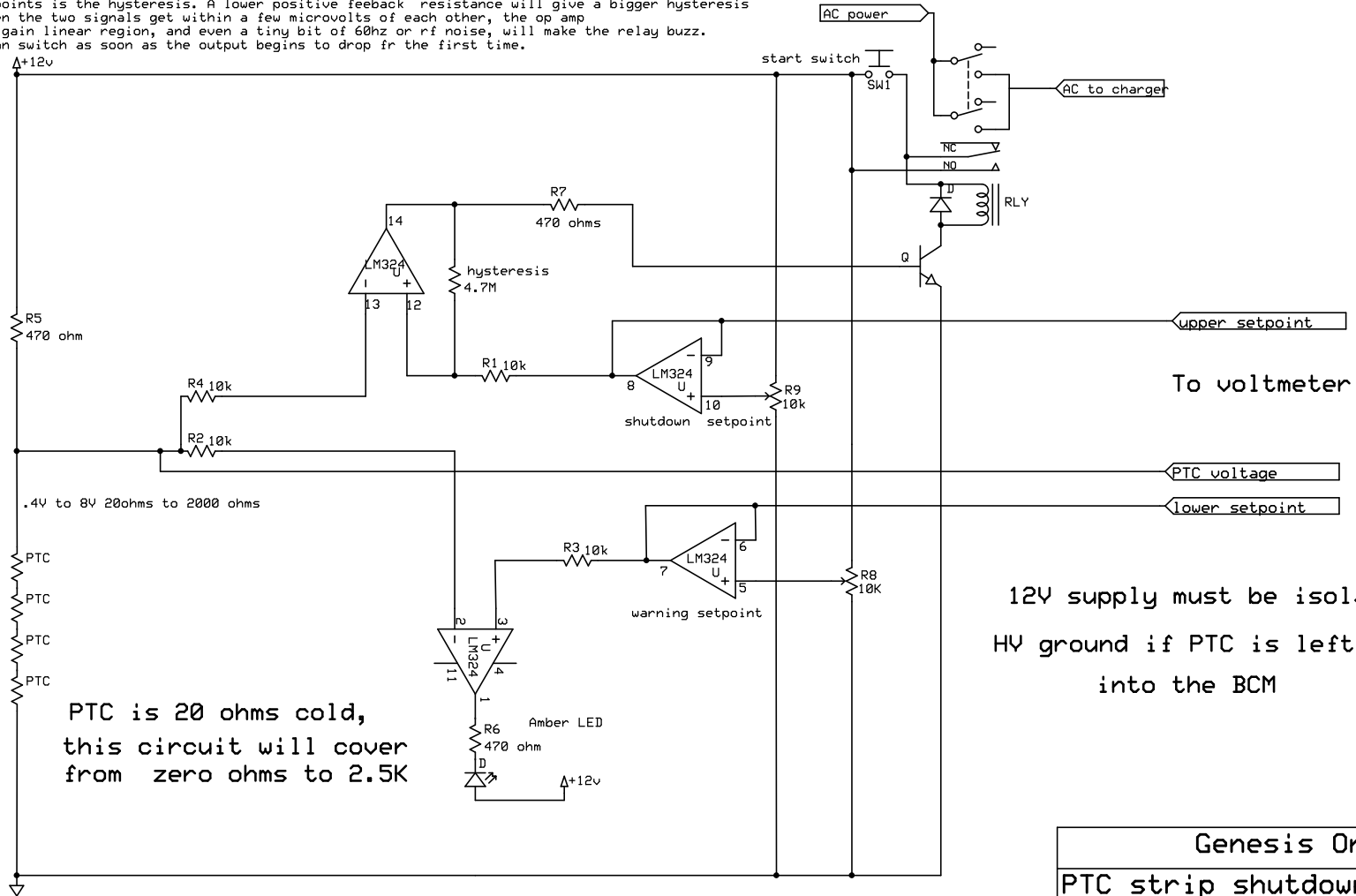


When output is high, the 4M resistor pulls the positive input slightly higher than the actual setpoint the PTC resistance/voltage has to raise to this slightly higher point before the op amp begins to switch off. as soon as it switches off, the 4M resistor now pulls the positive input a bit lower than the actual setpoint, firmly turning it off the difference in switchpoints is the hysteresis. A lower positive feedback resistance will give a bigger hysteresis without the feedback, when the two signals get within a few microvolts of each other, the op amp gets into its super high gain linear region, and even a tiny bit of 60hz or rf noise, will make the relay buzz. The feedback makes a clean switch as soon as the output begins to drop fr the first time.



PTC is 20 ohms cold, this circuit will cover from zero ohms to 2.5K

12V supply must be isolated from HV ground if PTC is left plugged into the BCM

Genesis One		
PTC strip shutdown circuit		
Designer's name	Rev 1.0 6/20/2010	Page # or name